

Cover Sheet for Submission of Maths Examinations Summer 2020

We would advise preparing your coversheets with your CID, Module Name and Code and Date, before the exams are due to take place.

CID: 01738166

Module Name: An Introduction to Applied Maths

Module Code: MATH40007

Date: 18/05/2020

Questions Answered (in the file):

Please tick next to the question or questions you have answered in this file.

Q1	
Q2	✓
Q3	
Q4	
Q5	
Q6	


(Note: this is a coversheet for all students - not all students will have exams with 6 questions. Please tick the boxes which are appropriate for your exam and/or the file you are submitting).

(Optional) Page Numbers for each question;

Page Number	Question Answered

If handwritten, please complete in CAPITAL Letters, in Blue or Black Ink, ensuring the cover sheet is legible.

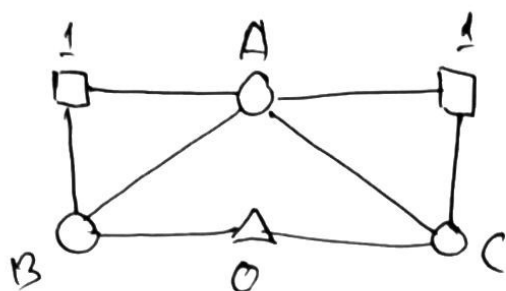- (a) The problem is equivalent to finding the potentials at nodes A, B and C when the square nodes have voltage 1 and the Δ is grounded (in a circuit).



By using the harmonic property of the potentials, each potential is the average of its neighbours \Rightarrow we get the equations:

$$A = \frac{1+1+C+B}{4} ; \quad \cancel{A = \frac{A+B+C}{3}} ; \quad \cancel{A = \frac{B+C}{2}}$$

$$C = \frac{A+1+0}{3} ; \quad B = \frac{A+1+0}{3} \Rightarrow 3B = A+1 \quad \Rightarrow 3C = A+1 \quad \Rightarrow \underline{B=C}$$

$$4A = 2 + 2B \Rightarrow B+1 = 2A, \text{ and } A = 3B-1 \Rightarrow$$

$$B+1 = 6B-2 \Rightarrow 5B=3 \Rightarrow \boxed{B=\frac{3}{5}} \quad \boxed{C=\frac{3}{5}}, \quad A = 3B-1 = \boxed{\frac{4}{5}=A}$$

\Rightarrow highest probability if he starts at A.


- (b) Let's denote P_A, P_B, P_C - probabilities that he reaches \square before Δ if he starts at A, B, C, respectively. We know from (a) that $P_A = \frac{4}{5}, P_B = P_C = \frac{3}{5}$.

If he starts at the Δ , then there is $\frac{1}{2}$ probability that he goes to C and $\frac{1}{2}$ to B. \Rightarrow

$$P_{esc} = \frac{1}{2} \cdot P_B + \frac{1}{2} P_C = \frac{1}{2} \cdot \frac{3}{5} + \frac{1}{2} \cdot \frac{3}{5} = \boxed{\frac{3}{5}}$$

Can also be calculated by $P_{esc} = \frac{C_{eff}}{2}$ when voltage at $\square = 1$ at $\Delta = 0$
 $2 \rightarrow$ nodes connected to Δ .

(c)

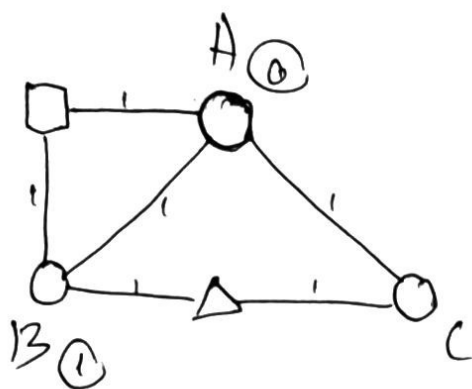


we have voltage at $A = 0$
 at $B = 1$.

$$P_{esc} = \frac{C_{eff}}{3} \rightarrow \text{effective conductance}$$

3 - nodes connected to A

Reduce graph:

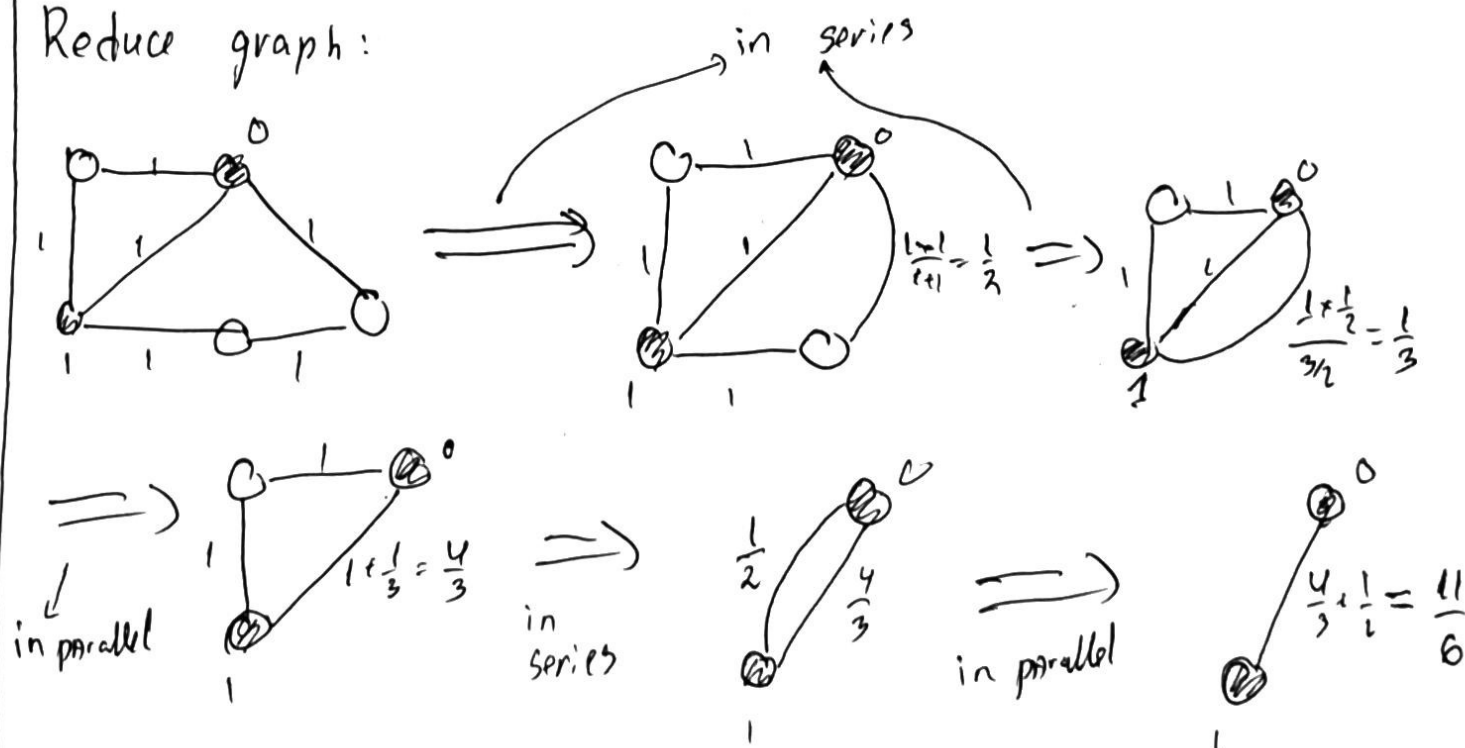

$$\Rightarrow C_{eff} = \frac{11}{6} \Rightarrow P_{esc} = \frac{11}{6} \cdot \frac{1}{3} = \boxed{\frac{11}{18}}$$